


PLC

**PROGRAMMABLE LOGIC
CONTROLLER**

Introduction to PLC

What is Relay ?

- Electromechanical switch

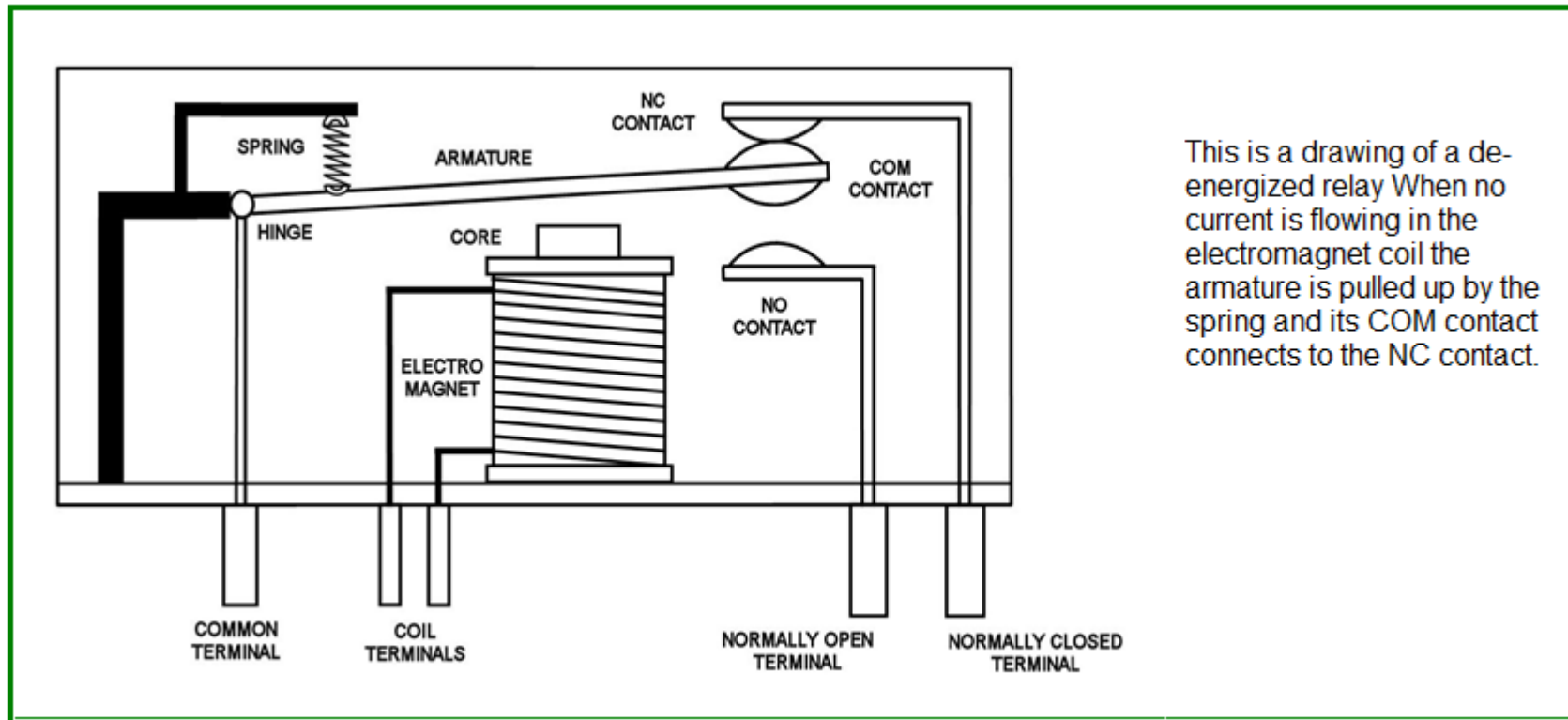

Introduction to PLC


Manufacturers

- Siemens (Top Manufacturer ~ 30% of the Market)
- Allen-Bradley
- Mitsubishi
- Others: Omron, Toshiba, HIMA, GE-Fanuc

Advantages

- Diverse range of Inputs/Outputs
- Protection from Electrical noise
- Protection from Vibration
- Diverse range of temperatures
- Input/Output Fast Scan Rates

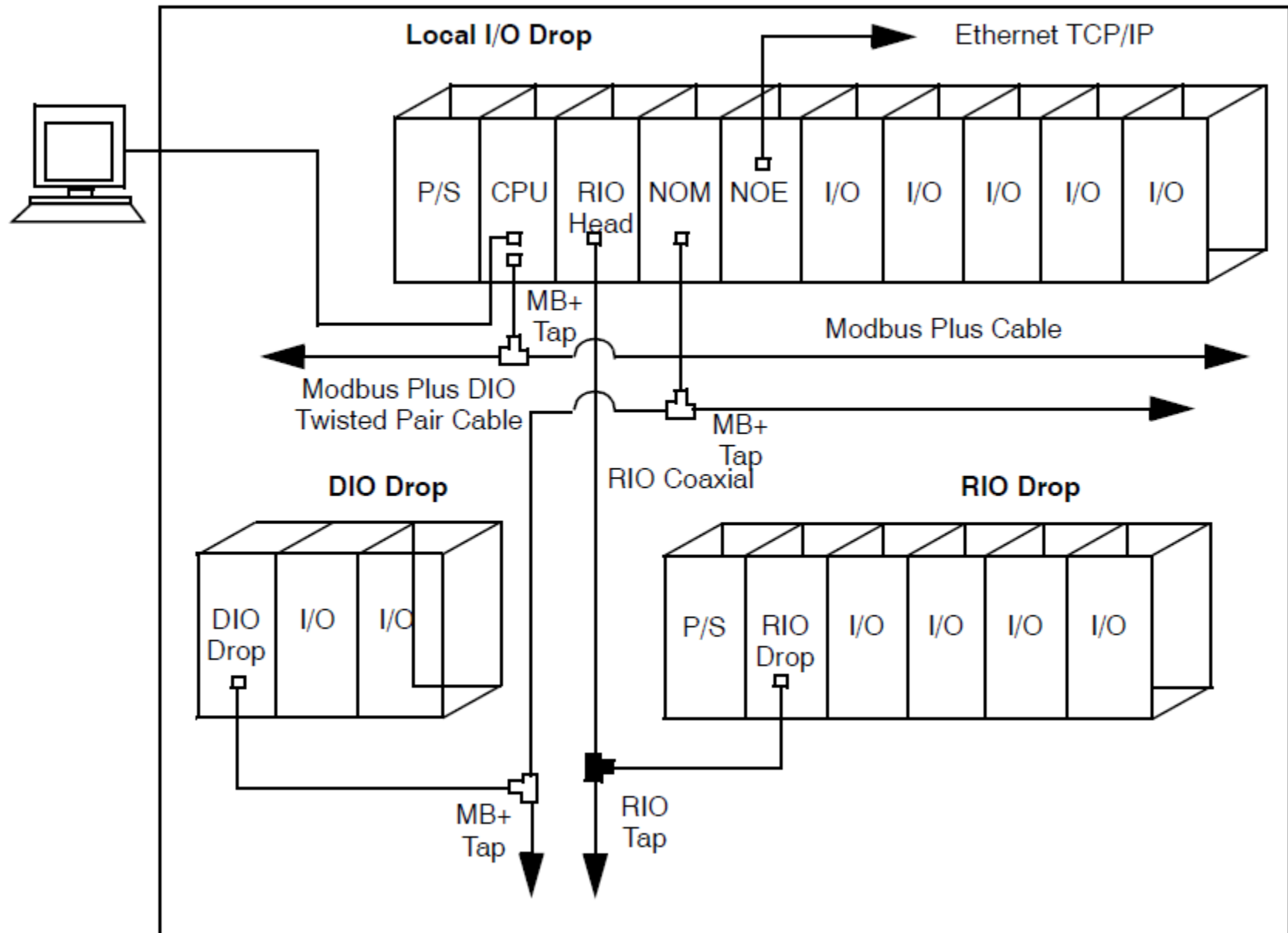Block Diagram of Modicon PLC (Schneider Electric)



Sensors and Actuators

▪ Example of Sensors

- Temperature
- Flow
- Pressure
- Level
- Limit switch
- On-off switch
- Pushbutton
- Fire/Gas/Smoke

▪ Example of Actuators

- Motors
- Valves
- Lamps/LEDs
- Alarms
- Pumps

Programming Methods


- Ladder Logic (most famous/widely used)
- Function Blocks (new trend)
- Other: Sequential Function Charts, Structured Text

Programming Devices

- Hand held Programmers
- PCs Off-line Programming
- Dedicated Programmers



Introduction to Ladder Logic

- Basic Building Block: Relay

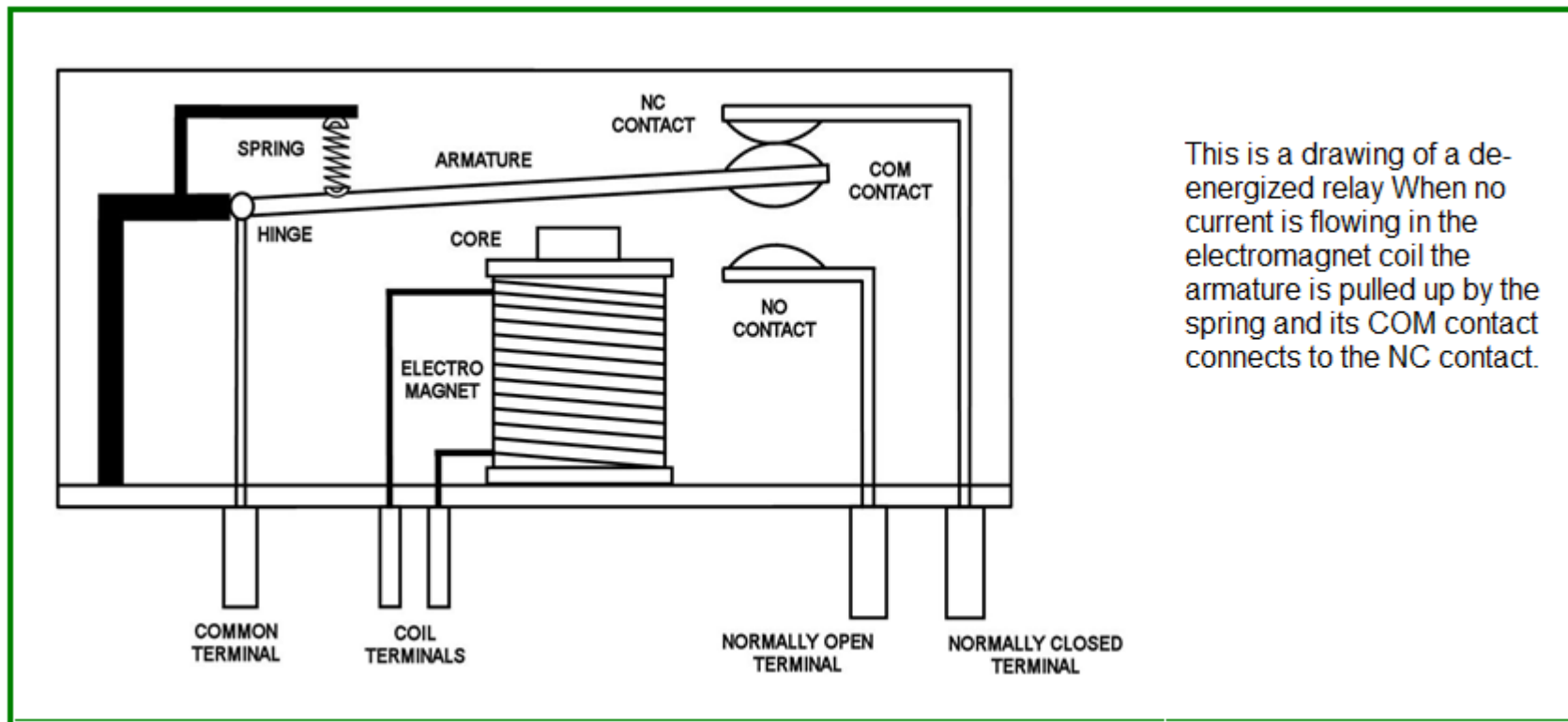

Introduction to Ladder Logic

■ Programming Symbols and Terminology

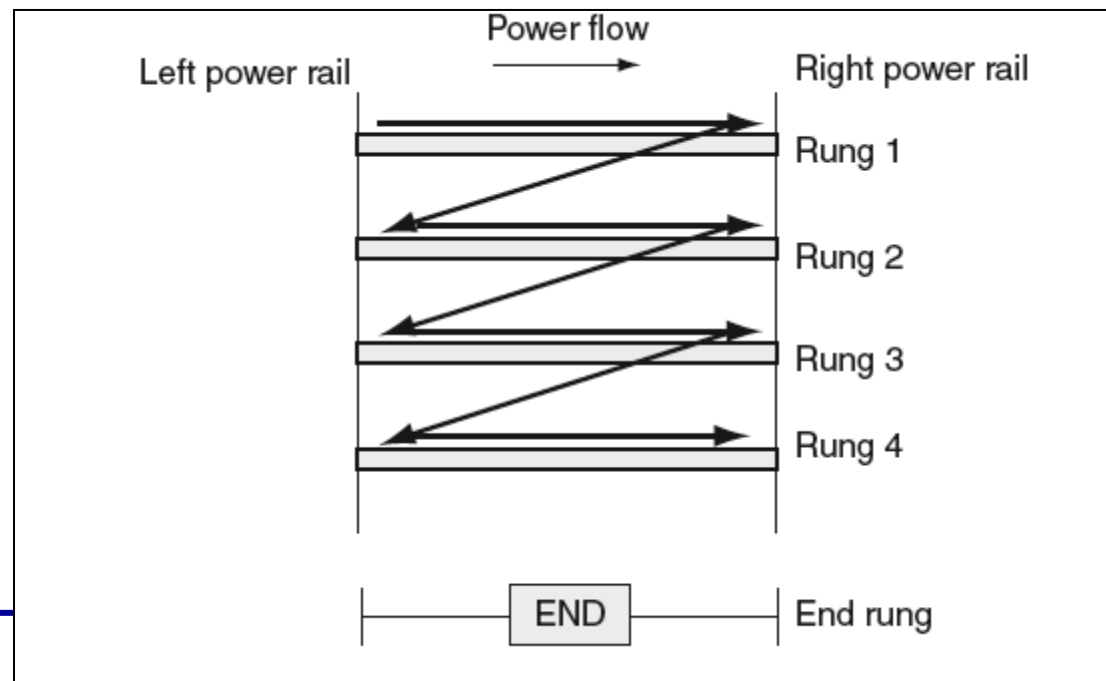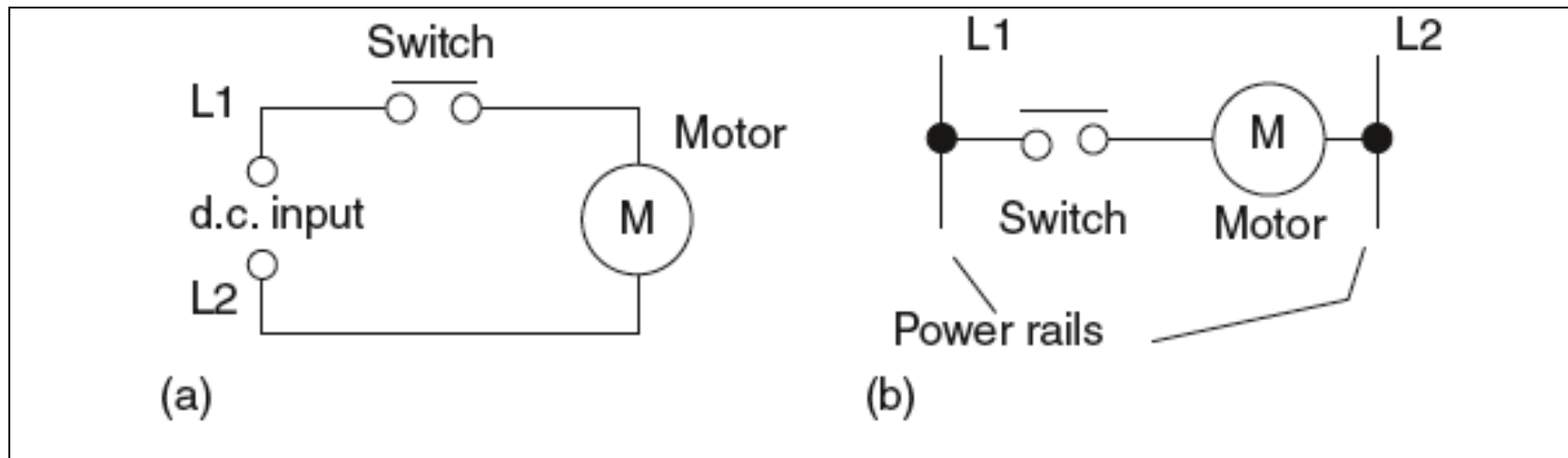


Introduction to Ladder Logic

- International Electro-technical Commission Standard (IEC 1131-3)

A horizontal link along which power can flow



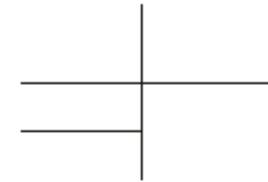Interconnection of horizontal and vertical power flows



Left-hand power connection of a ladder rung



Right hand power connection of a ladder rung




Normally open contact



Normally closed contact





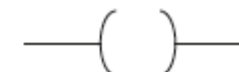Output coil: if the power flow to it is on then the coil state is on



Ladder Logic - Addressing

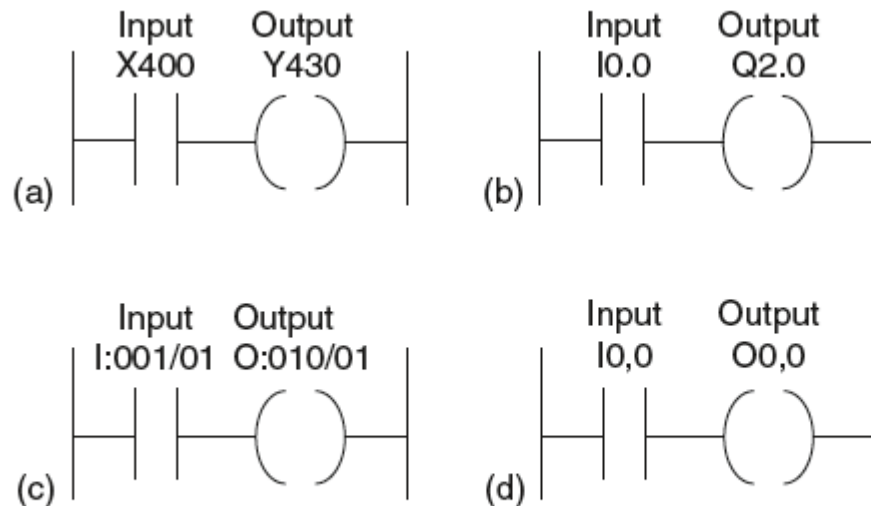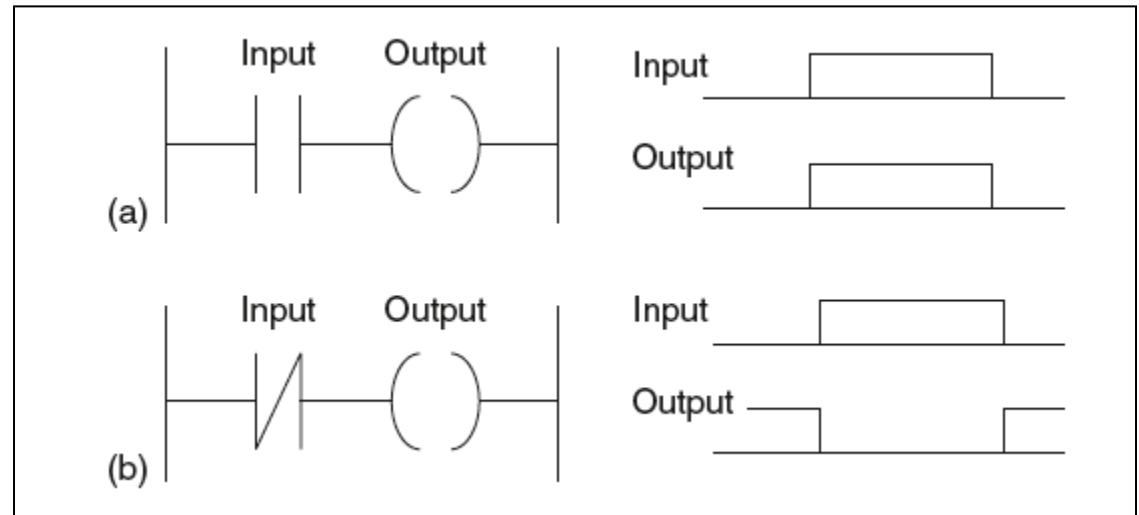- Inputs and Outputs are all identified by their addresses
(notation depend on manufacturer)



Notation: (a) Mitsubishi (b) Siemens (c) Allen-Bradley (d) Telemecanique

Example – Automated Car Park Entrance

- Problem Statement

- Develop the Ladder Logic for an Automated Entry to a Car Parking using IR sensor for Car Detection and Motorized Barrier Beam.

- Inputs / Outputs

- How many sensors and actuators??

- **LadSim Software:**

Fully functional ladder logic design and PLC simulation software program by BYTRONIC that incorporates the functions used in PLC ladder programming. LADSIM uses the PC as a virtual PLC.


**16 inputs/16 outputs/16 flags(Auxiliary Relays)/8 timers/
8 counters/4 16-Shift Bit Registers.**

Example – Automated Car Park Entrance



Automated Car Park Entrance

- Do not forget Resetting your timers !

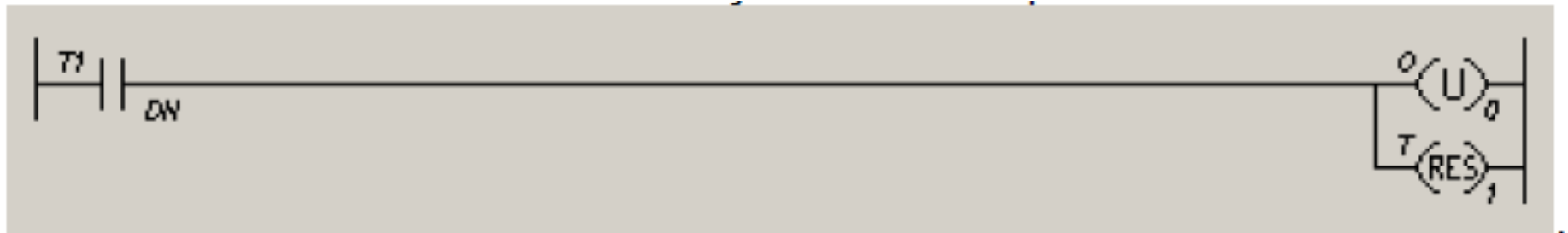

Adding counters

- For example: 6 cars means car park full light is ON



PLC – Advanced Topics

- Safety
 - Fail-Safe
- Redundancy (Safety Integrity Level – SIL)
 - IEC Standard 61508/61511 (Application of Safety Instrumented Control Systems in the Process Industry)

Lab # 1 – Conveyor Belt

- It is required to design a Ladder Logic diagram to control the operation of a conveyor belt.
- There is a switch to start the system initially. The required operation is as follows: when the system is ON the conveyor belt starts moving with items loaded on it
- After 3 seconds the belt stops and the first item is inspected by a human inspector who stands before the belt and visually detects the passing items, the visual inspection takes about 5 seconds to detect if the item is good or not.
- After the 5 seconds the conveyor belt continues moving again. The time required for the next item to arrive before the inspector is 3 seconds. The inspector can reject items using a push button; after the item is rejected the conveyor belt continues moving directly without waiting the 5 seconds to pass.
- After the inspector rejects 3 items the system should stop.

QUESTIONS?

**Note: Lab#1 Due Date is Sunday
9th October**